
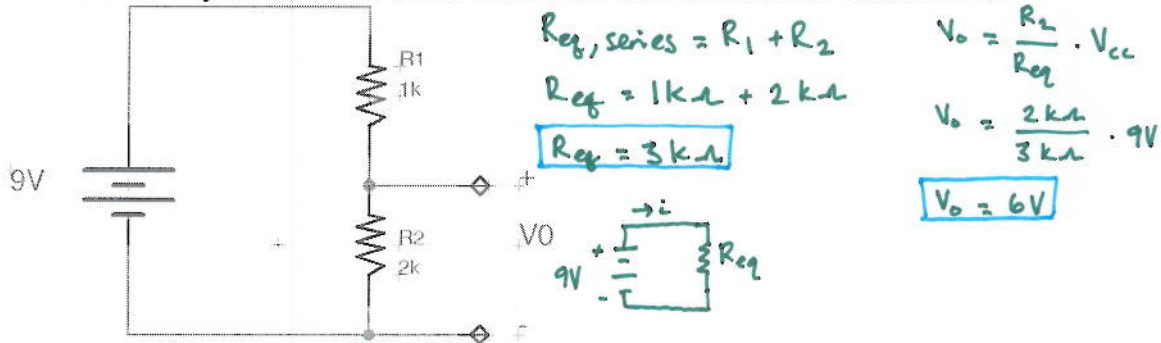


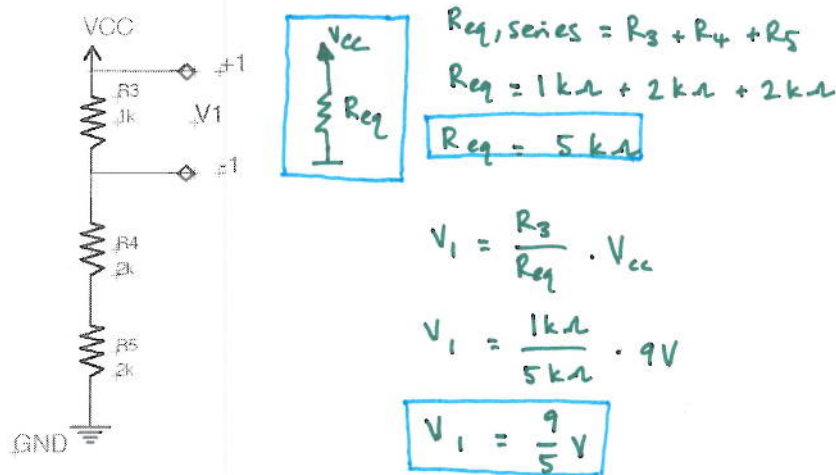
1. (1 pt.) Using Ohm's Law, find the value of  $V_0$ . All resistances are in Ohms ( $\Omega$ ), be sure to include units in your answers! Note: all k's are short for  $k\Omega$  for rest of HW.




2. (2 pts.) Draw the equivalent circuit using only one resistor ( $R_{eq}$ ), and find its value. Then find the value of  $V_1$ . Assume that  $V_{CC} = 9V$  for the rest of the HW.



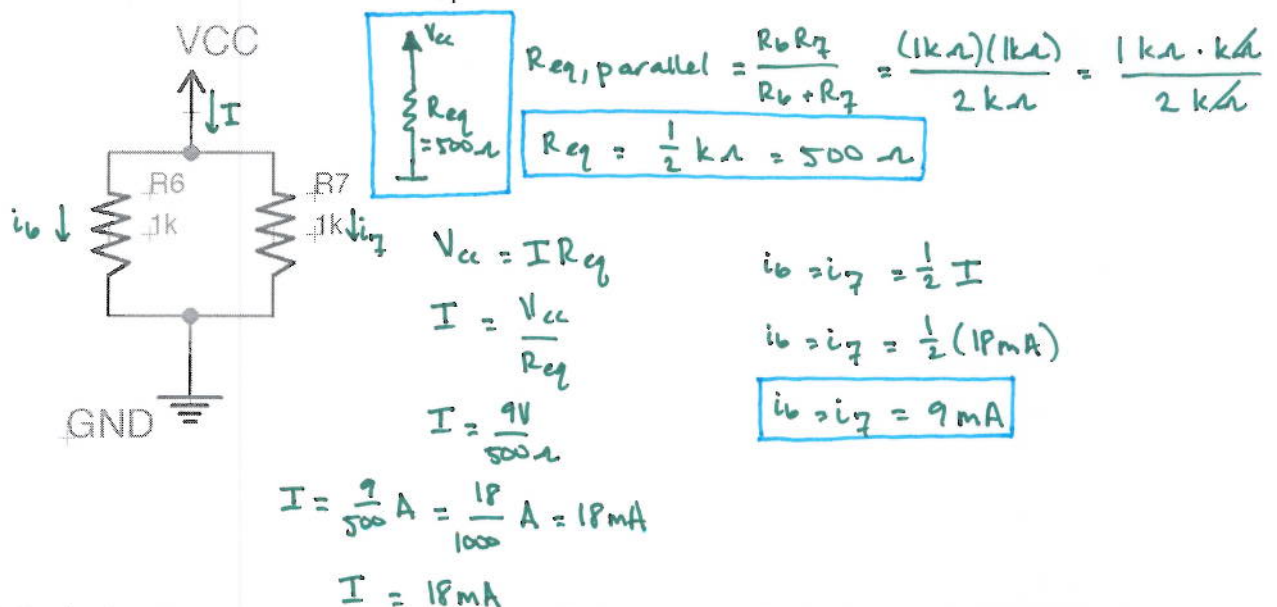
3. (2 pts.) Find the current that flows through each  $R_6$  and  $R_7$ . Then draw the equivalent one resistor circuit and label the value of  $R_{eq}$ .



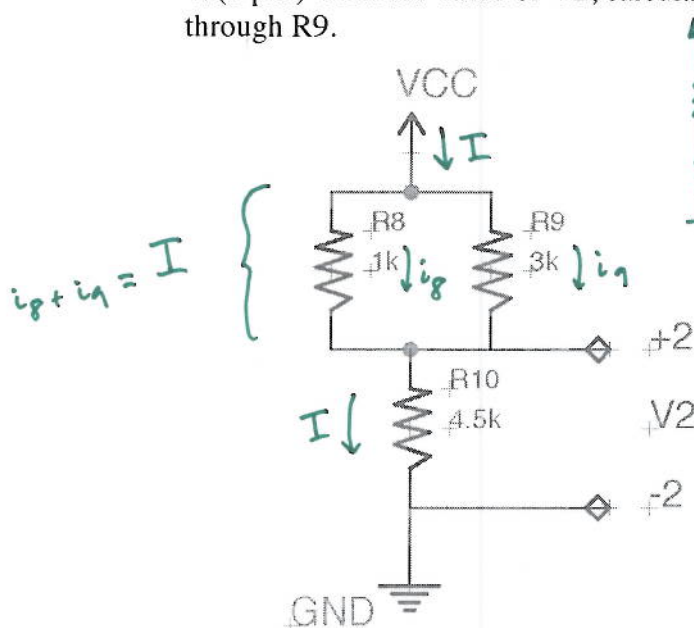
4. (3 pts.) Find the value of  $V_2$ , calculate  $R_{eq}$  for the entire circuit, find the current that flows through  $R_9$ .



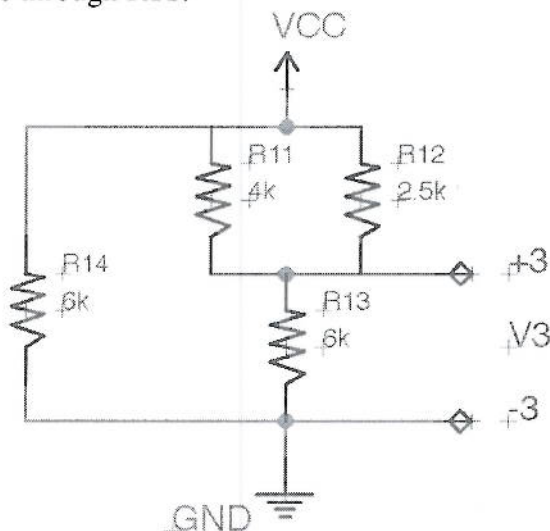5. CQ (optional) (3 pts.) Find  $R_{eq}$  for the entire circuit, calculate  $V_3$ , and find the current that flows through  $R_{11}$ .



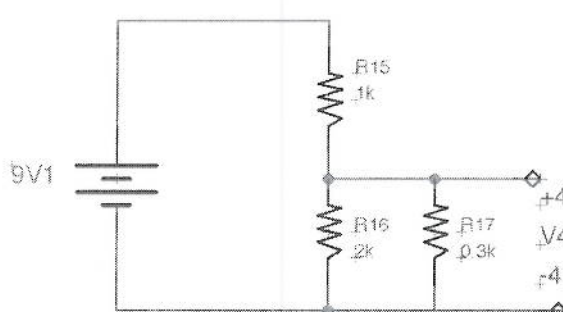6. (2 pts.) Find the value of  $V_4$ . What would happen to  $V_4$  if  $R_{17} = 30\Omega$ ?  $5\Omega$ ?



$$R_{eq} = \frac{R_{16} \cdot R_{17}}{R_{16} + R_{17}}$$



$$V_4 = V_{cc} \cdot \frac{R_{eq}}{R_{eq} + R_{15}}$$

$$R_{eq}(R_{17} = 0.3k\Omega) = \frac{2k\Omega \cdot 0.3k\Omega}{2k\Omega + 0.3k\Omega} = 260.87\Omega \rightarrow V_4 = 1.862V$$

$$R_{eq}(R_{17} = 30\Omega) = \frac{(2k\Omega) \cdot (30\Omega)}{2k\Omega + 30\Omega} = 29.5567\Omega \rightarrow V_4 = 0.258V$$


$$R_{eq}(R_{17} = 5\Omega) = \frac{2k\Omega \cdot 5\Omega}{2k\Omega + 5\Omega} = 4.98753\Omega \rightarrow V_4 = 0.0446V$$

5.

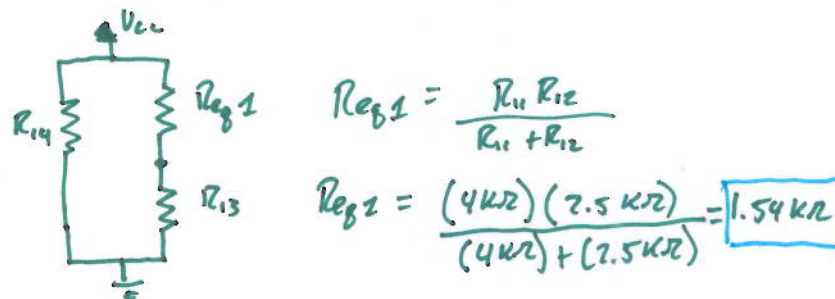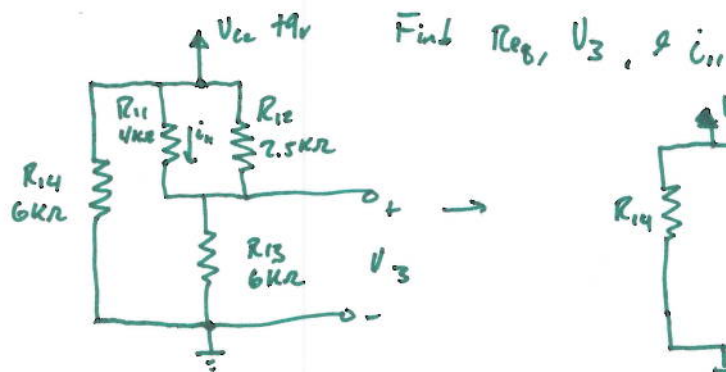

$$R_{eq1} = \frac{R_{11} R_{12}}{R_{11} + R_{12}}$$
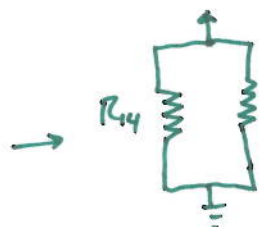
$$R_{eq2} = \frac{(4k\Omega)(2.5k\Omega)}{(4k\Omega) + (2.5k\Omega)} = 1.54k\Omega$$



$$R_{eq2} = R_{eq1} + R_{13}$$

$$R_{eq2} = \frac{R_{11} R_{12}}{R_{11} + R_{12}} + R_{13}$$

$$R_{eqT} = \frac{R_{eq2} R_{14}}{R_{eq2} + R_{14}}$$

$$R_{eq2} = (1.54k\Omega) + (6k\Omega)$$

$$R_{eq2} = 7.54k\Omega$$

$$R_{eqT} = \frac{(7.54k\Omega)(6k\Omega)}{(7.54k\Omega) + (6k\Omega)}$$

$$R_{eqT} = 3.34k\Omega$$

$$R_{eqT} = \frac{\left( \frac{R_{11} R_{12}}{R_{11} + R_{12}} + R_{13} \right) R_{14}}{\left( \frac{R_{11} R_{12}}{R_{11} + R_{12}} + R_{13} \right) + R_{14}}$$

b.  $V_3$


$$V_3 = V_{cc} \frac{R_{13}}{R_{13} + R_{eq2}}$$

$$V_3 = V_{cc} \frac{R_{13}}{R_{13} + \left( \frac{R_{11} R_{12}}{R_{11} + R_{12}} \right)}$$

$$V_3 = 9V \cdot \frac{(6k\Omega)}{(6k\Omega) + (1.54k\Omega)}$$

$$V_3 = 7.16V$$

c.  $i_{in}$

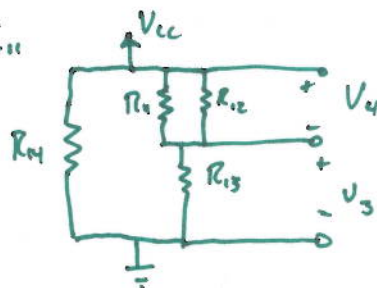

$$V_{cc} = V_4 + V_3$$

$$V_4 = V_{cc} - V_3$$

$$V = IR$$

$$V_4 = i_{in} R_{11}$$

$$i_{in} = \frac{V_4}{R_{11}}$$

$$i_{in} = \frac{(V_{cc} - V_3)}{R_{11}}$$

$$i_{in} = \frac{(9V) - (7.16V)}{(4k\Omega)}$$

$$i_{in} = 0.46mA$$